
## Mathematical Modelling - Assignment 6: Solving a 2<sup>nd</sup>-order DE with Matlab and Simulink.

Extra information: Sometimes you would like to select a single row or a single column form a matrix. Matlab offers a way to do it.

Try: M = rand(2,5)
row1 = M(1,:)
column2 = M(:,2)

## Assignment 1: Solving a 2nd-order DE with Matlab

Given is the following RLC-circuit:

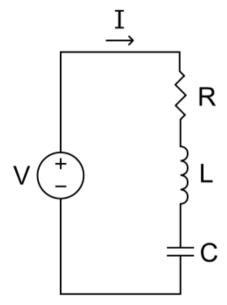

[reference: https://en.wikipedia.org/wiki/RLC\_circuit]

In case of a DC-Voltage source, the differential equation belonging to this circuit is equal to

$$\frac{d^2I(t)}{dt^2} + \frac{R}{L}\frac{dI(t)}{dt} + \frac{1}{LC}I(t) = 0$$

The theoretical derivation of this differential equation can be found in the Wikipedia reference given above.


(a) Rewrite this second-order differential equation to a system of two first-order equations.

$$\begin{pmatrix} \frac{dz1}{dt} \\ \frac{dz2}{dt} \end{pmatrix} = \begin{pmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{pmatrix} \begin{pmatrix} z1 \\ z2 \end{pmatrix}$$

(b)


Given is 
$$L=1$$
 H,  $C=1$ F,  $I(0)=0$  A,  $\frac{dI(t)}{dt}\Big|_{t=0}=4$ A/s

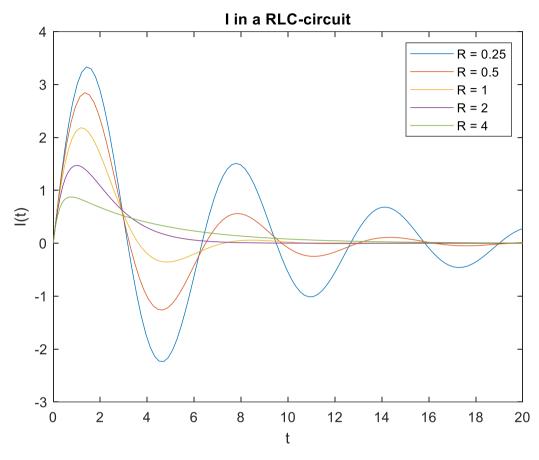Make a plot of the current I(t) for the time period from t = 0 to 20 seconds, using five different resistor values of R being 0.25  $\Omega$ , 0.5  $\Omega$ , 1  $\Omega$ , 2  $\Omega$  and 4  $\Omega$ , using the Matlab command ode45. Plot the results for the different resistor values together in one single graph. Don't forget to use a title, correct labels for the x- and y-axis and a legend too.


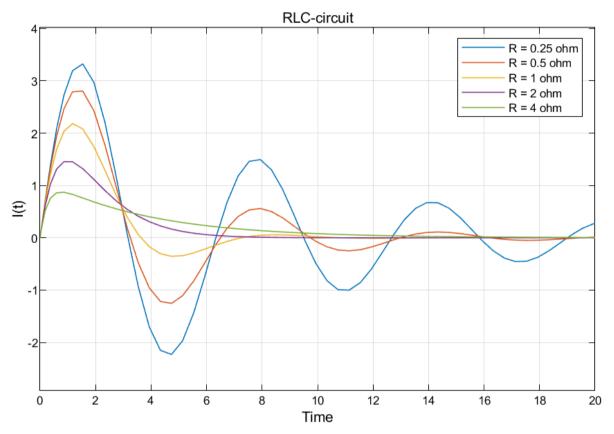
## Assignment 2: Solving a 2nd-order DE with Simulink.

Solve assignment 1 by making a Simulink model instead of. solving it by Matlab code. To implement the model, you should use summation blocks, integrating blocks and/or gain blocks as well as a scope and input sources. Plot the results for the different resistor values together in one single scope. Make use of a legend in the scope. Finally, check of you obtain the same result as in assignment 1.



The Simulink graphs are the same as the Matlab graphs.